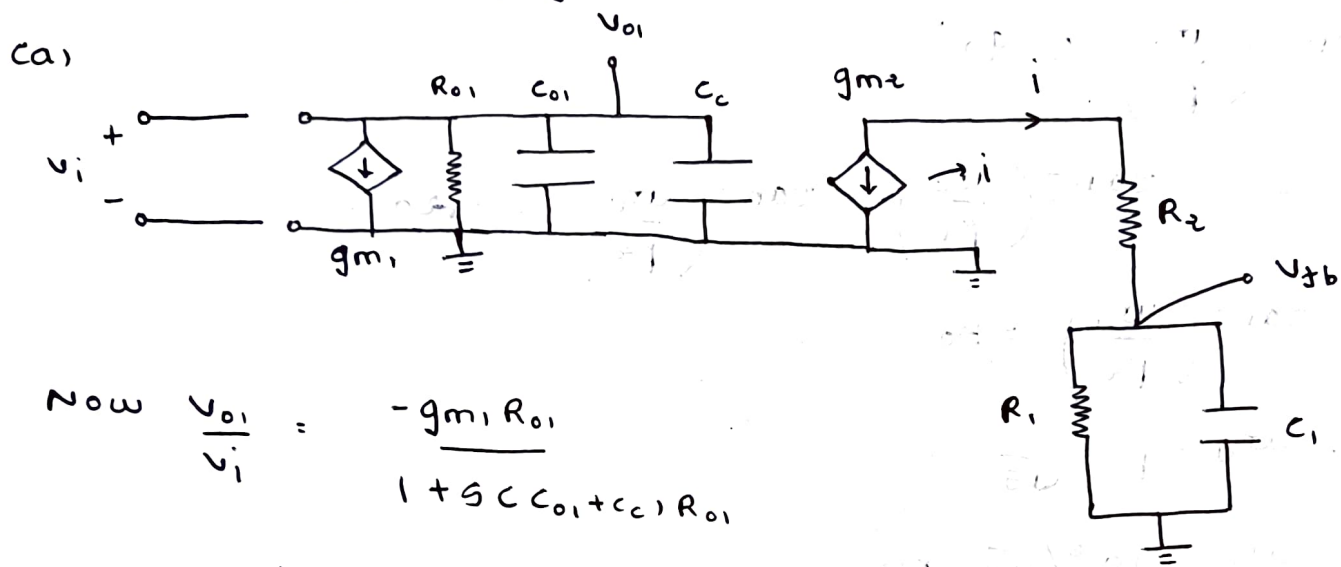


① we have; for loop gain



$$\text{Now } \frac{V_{01}}{V_i} = \frac{-g_{m1} R_{01}}{1 + s(C_{01} + C_c) R_{01}}$$

$$\text{Now; } \frac{i}{V_i} = \frac{g_{m1} g_{m2} R_{01}}{1 + s(C_{01} + C_c) R_{01}}$$

$$Z = \frac{\frac{R_1}{sC_1}}{R_1 + \frac{1}{sC_1}} = \frac{R_1}{1 + sC_1 R_1}$$

$$\therefore V_{fb} = i Z$$

$$\therefore \frac{V_{fb}}{V_i} = \frac{g_{m1} g_{m2} R_{01}}{(1 + s(C_{01} + C_c) R_{01})} \times \frac{R_1}{(1 + sC_1 R_1)}$$

$$\therefore LG(s) = \frac{g_{m1} g_{m2} R_{01} R_1}{(1 + s(C_{01} + C_c) R_{01}) (1 + sC_1 R_1)}$$

$$= \frac{10^5}{10^6}$$

$$(1 + \frac{s}{10^6}) (1 + s(10pF + C_c) 10^5)$$

$$=$$

cb) Now for PM of 60° ;

$$\angle LG = -120^\circ$$

\therefore Now by dominant pole compⁿ; $p_1 \ll p_2$

$$\therefore \tan^{-1}\left(\frac{\omega_0}{p_1}\right) \approx 90^\circ$$

$$\therefore \text{Now, } -\tan^{-1}\left(\frac{\omega_0}{p_1}\right) - \tan^{-1}\left(\frac{\omega_0}{p_2}\right) = -120^\circ$$

$$\therefore \tan^{-1}\left(\frac{\omega_0}{p_2}\right) = 30^\circ$$

$$\therefore \omega_0 = p_2 / \sqrt{3}$$

$$\therefore \omega_0 = 10^6 / \sqrt{3} \text{ r/s}$$

$$= 577.35 \text{ Kr/s}$$

$$\therefore \text{Now, } \omega_0 = \frac{10^5}{10^5 (10pF + C_c)}$$

$$\therefore 10pF + C_c = 1.732 \mu F$$

$$\therefore C_c = 1.732 \mu F$$


$$H \equiv LG$$

$$\omega_1 = 5.774 \text{ r/s}$$


$$\omega_0 = 577.35 \text{ Kr/s}$$

$$\omega_2 = 10^6 \text{ r/s}$$


cc) Bode plots are:

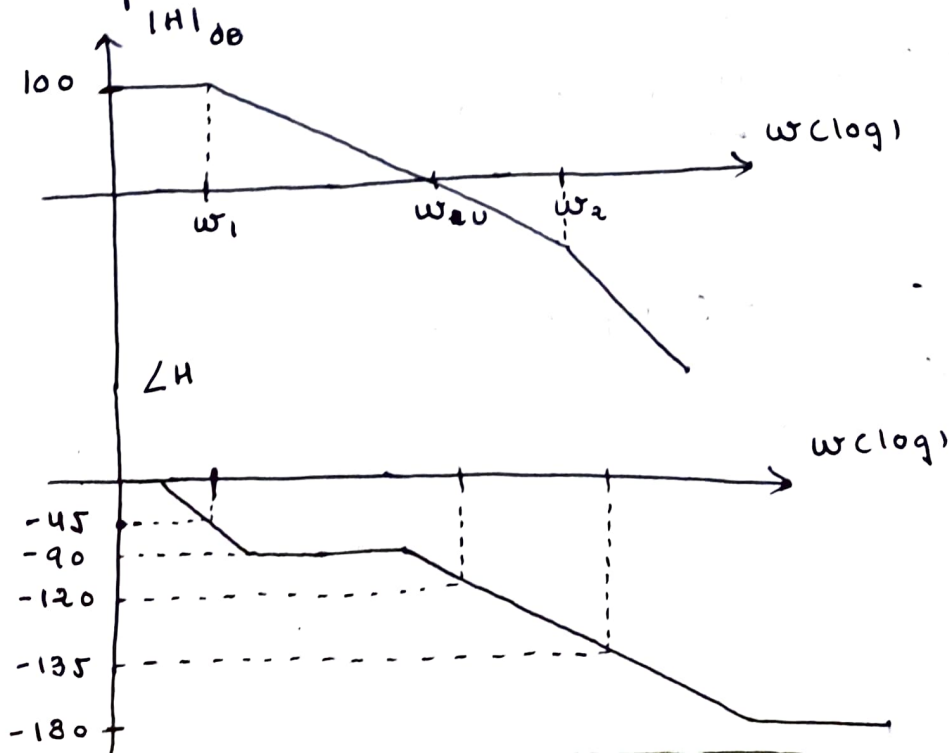

② We have

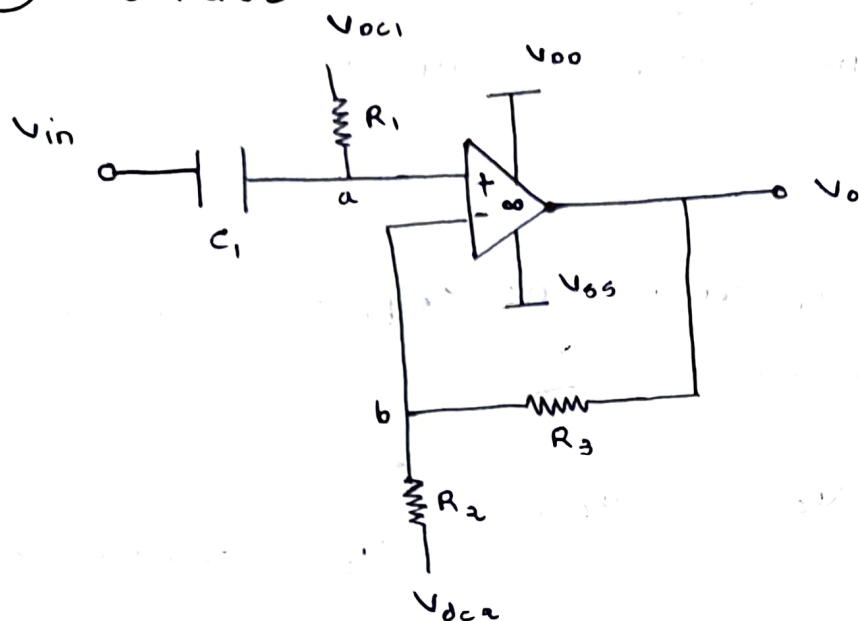

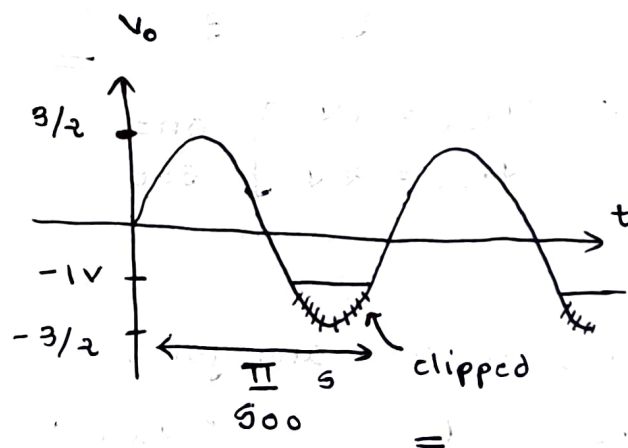Case Now; $V_{in} = \sin 1000t \text{ V}$
 $C_1 \rightarrow \infty$
 $\therefore \frac{1}{j\omega C_1} \rightarrow 0 \text{ (S.C.)}$
 $V_{dc1} = V_{dc2} = 0 \text{ V}$



Now in ac analysis;

$$V_o = V_{in} \left(1 + \frac{R_3}{R_2} \right) \quad \text{or;}$$

$$V_o \left(\frac{2}{3} \right) = V_{in}$$

$$\therefore V_o = \frac{3V_{in}}{2} = \frac{3}{2} \sin 1000t \text{ V} \quad \begin{matrix} \nearrow \text{due to} \\ V_{ss} = -1 \text{ V} \end{matrix}$$

= ideally but..

$$\frac{V_{dc2} (2)}{3}$$

$$\frac{V_{dc2}}{3}$$

Now for proper functioning of device;

In dc case $(V_o)_{dc} = 0 \text{ V}$

$$V_b = +V_{dc2} \left(\frac{2}{3} \right) = V_{dc1}$$

$$\therefore 3V_{dc1} + 2V_{dc2} = 0 \text{ V} \quad \times$$

$$V_{dc2} = 3V_{dc1}$$

One set, $\left\{ \begin{matrix} V_{dc1} = 1 \text{ V} \\ V_{dc2} = 3 \text{ V} \end{matrix} \right\}$

Let But to avoid C_1 from charging;

$$V_{dc1} = V_{dc2} = \underline{0V} \text{ is most usable (WRONG!)}$$

Now; we can But;

For proper functioning of circuit; no clipping as in cal;
 $(V_{oldc} = 0.5V \text{ (for cal case)})$

$$\text{Now; } - \left(\frac{V_{dc2} - 0.5}{3} \right)^2 + V_{dc2} = V_{dc1}$$

$$V_o = 0.5 + 1.5 \sin$$

$$(1000t) V$$

$$\frac{V_{dc2}}{3} + \frac{1}{3} = V_{dc1}$$

no clipping

$$\left. \begin{array}{l} V_{dc1} = 1V \\ V_{dc2} = 2V \end{array} \right\} \text{one set}$$

cc) Now; In, AC analysis;

$$\bar{V}_a = \frac{R_1}{R_1 + sC_1 R_1} \bar{V}_{in}$$

$$= \left(\frac{R_1}{R_1 + \frac{1}{sC_1}} \right) \bar{V}_{in}$$

$$s = j\omega$$

$$\therefore C_1 \gg 100nF$$

$$\text{One value; } C_1 = 1\mu F$$

$$= \left(\frac{j\omega C_1 R_1}{j\omega C_1 R_1 + 1} \right) \bar{V}_{in}$$

$$\therefore \text{At; } \omega = 1000 \text{ rad/s; } |z| \approx 1$$

$$\therefore \omega C_1 R_1 \gg 1$$

$$\therefore C_1 \gg \frac{1}{\omega R_1} (= 100nF)$$

(b) For proper functioning; no clipping

$$\therefore V_{oldc} = A_{in} \cdot 3A$$

$$\therefore -\frac{3A_{in}}{2} + V_{oldc} = -1V$$

$$\therefore V_{oldc} = \frac{3A_{in}}{2} - 1V$$

$$\therefore V_b = V_{dc2} - \left(\frac{V_{dc2} - V_o}{3} \right)^2$$

$$= \frac{V_{dc2} + 2V_o}{3}$$

$$= \frac{V_{dc2} + 3A_{in} - 2}{3}$$

$$\therefore V_{dc1} = \frac{V_{dc2} + 3A_{in} - 2}{3}$$

$$\therefore 3V_{dc1} = V_{dc2} + 3A_{in} - 2$$

Any set would work
depending on A_{in}

cd) Now for max
 A_{in} for proper
working;

$$3A_{in}^m - 1 = 4$$

$$A_{in}^{max} = \frac{5}{3} V$$

$$\textcircled{3} \text{ Now; } Z_1 = \frac{1}{G_m + 2}$$

$$= \frac{1}{2}$$

$$\therefore Z_1 = \frac{5s^2 + 2}{50s^2 + 2 \cdot 5s + 20}$$

$$\frac{1}{Z_1} = \frac{Z}{-}$$

$$\therefore Z = 10 + \frac{5/2}{5s + \frac{2}{5}}$$


$$Z = \frac{50s^2 + 2 \cdot 5s + 20}{5s^2 + 2}$$

$$= 10 + \frac{2 \cdot 5s}{5s^2 + 2}$$

$$\frac{1}{Z_1} = 10 + \frac{(5s)(1/2s)}{5s + 1/2s}$$

$$= \left(\frac{1}{10}\right)^{-1} + \frac{1}{\left(\frac{1}{2s} + 5s\right)^{-1}}$$
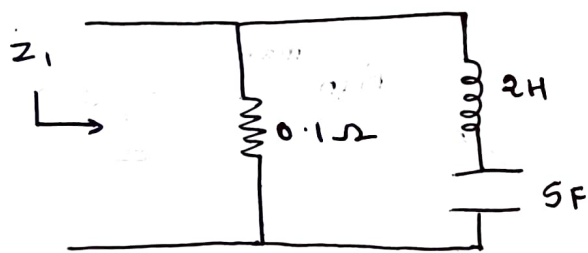
$$= \left(\frac{1}{10}\right)^{-1} + \frac{1}{2s + \frac{1}{5s}}$$



=


④ Now, we have

$$i_L = \frac{V_{in} - V_o}{5L}$$

$$i_C = (V_{in} - V_o) 5C$$


$$V_C = V_{in} - V_o$$

$$R_{iL} = \frac{V_{in} - V_o}{5L/R}$$

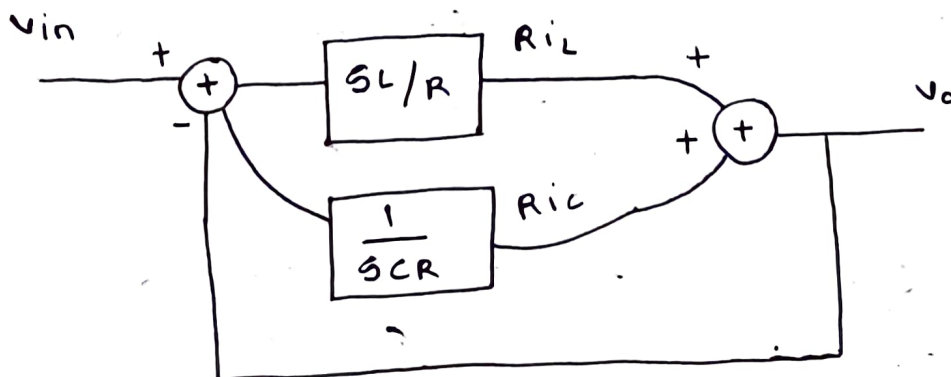

Block diagram

∴ Now;

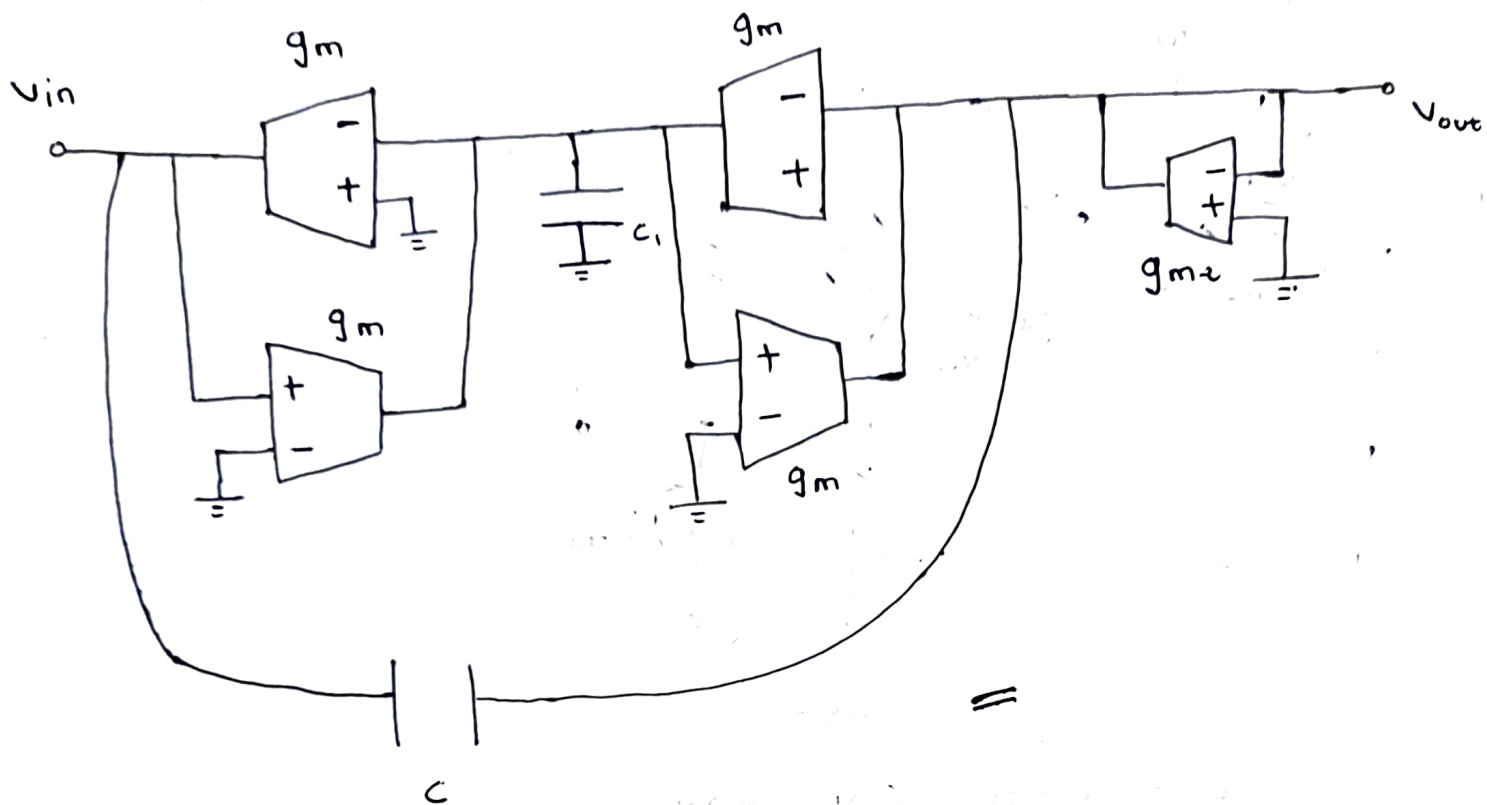

∴ Now; $\frac{C_1}{g_{m1}} = 1 \mu\text{H} \rightarrow 1 \text{ set} \left\{ \begin{array}{l} g_m = 1 \text{ S A/V} \\ C_1 = 1 \text{ pF} \end{array} \right.$

$C = 1 \text{ pF}$

$g_{m2} = 0.02 \text{ S A/V}$

=

⑥ Now; $V_{in} = 0.775 \text{ V}$

(a) $b_2 = 1$
 $b_1 = 1$
 $b_0 = 0$

Output = 110


(b) Now for 'ca' case;

$V_{th2} = 0.76 \text{ V}$

$V_{th3} = 0.857 \text{ V}$

=

5) we now have;

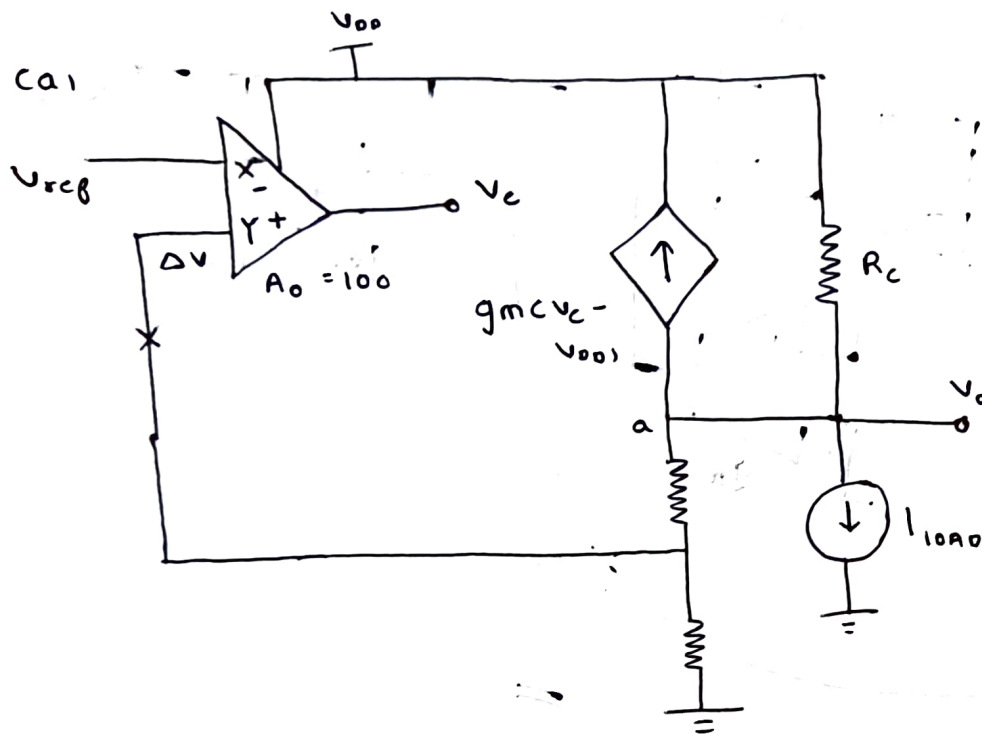

For $-V_c$ b.b. operation; ($V_{DD} \equiv 0V$)

Now KCL @ a; ($I_{LOAD} \equiv 0A$)

$$g_m(V_c) + \frac{V_0}{R_c} + \frac{V_0}{R_1 + R_2} = 0$$

$$V_c = A V_c$$

$$V_0 \left[\frac{1}{R_c} + \frac{1}{R_1 + R_2} \right] = -g_m A \Delta V$$

$$V_0 < 0$$

$$V_0 \left(\frac{R_2}{R_1 + R_2} \right) < 0$$

Signs flipped; assumption is correct

$$\begin{array}{c|c} X & - \\ \hline Y & + \end{array}$$

=

(b) We have;

KCL @ a;

$$-0.5 \text{ mA}$$

$$1 \text{ mS}(V_c - 2.5) + \cancel{2 \text{ mA}} + 1 \text{ mA} + 0.1 \text{ mA} = 0$$

$$V_c = \cancel{-0.6 \text{ V}} \quad 1.9 \text{ V}$$

$$\text{Now; } 100(V_y - V_x) = \cancel{-0.6} \quad 1.9$$

$$V_y - V_x = \cancel{-6 \text{ mV}} \quad 19 \text{ mV}$$

$$1 \text{ V} - V_x = \cancel{-6 \text{ mV}} \quad 19 \text{ mV}$$

$$0.981$$

$$V_x = \cancel{1.006 \text{ V}} \quad (= V_{ref})$$

=

(c) Now Keeping V_{ref} constant;

$$\therefore (V_o)_{ideal} = \cancel{2.012 \text{ V}} \quad 1.962 \text{ V}$$

$$\therefore \text{Abs error} = \cancel{12 \text{ mV}} \quad 38 \text{ mV}$$

=

(d) Now; For Z_o ;

$$V_{ref} = 0 \text{ V}; V_{DD} = 2.5 \text{ V}$$

$$\text{Now; } V_c = 100 V_t$$

KCL @ a;

$$\frac{(V_t - 2.5)}{1 \text{ K}} + 1 \text{ mS}(100 V_t - 2.5) + \frac{V_t}{20 \text{ K}} + \frac{V_t}{2 \text{ K}} = i_t$$

(Wrong!)

$$\text{Now; } V_{ref} = V_{DD} = 0 \text{ V}$$

$$V_c = 0 \text{ V}$$

$$\therefore Z_t = 645.161 \Omega$$

=

$$\frac{V_t}{1 \text{ K}} + \frac{V_t}{20 \text{ K}} + \frac{V_t}{2 \text{ K}} = i_t$$